New **FREED** Components for HI-FIDELITY Amplifier Provide IMPROVED PERFORMANCE



This Freed circuit incorporates several changes from the original Williamson circuit to provide optimum performance at high and low frequency extremes. It is rated at 10 watts with triode connected output tubes. However, by connecting the screen grids of these tubes to taps provided on the Freed KA-10 output transformer, it is possible to double the power output for a given distortion percentage.

Values of the two feedback resistors (R_{11} and R_{12}) are chosen to provide 20 db of negative feedback from the 16 ohm tap. If it is desired to change the screen feedback arrangement, R_{12} , R_{23} and R_{24} should be removed. The screen grids of V_3 and V_4 are then connected to the taps provided on the primary of transformer T_2 .

Recommended power supply is choke-input type with a two-section L-C filter to maintain constant D.C. output and to improve filtering to the voltage amplifiers.


The required 550 volts AC for the rectifier can be furnished by a Freed KP-10 power transformer.

Filtering is provided by Freed KC-10 and KC-11 filter reactors and the 20 mfd, filter condensers.


In construction, all grounds should be made to a common bus wire which is tied to the chassis at only one point (the input jack). Filament leads should be twisted and routed away from all grid leads. Filaments should be grounded through a center tap on the filament winding, or a 100 chm potentiometer across the winding.

The completed amplifier requires three adjustments:

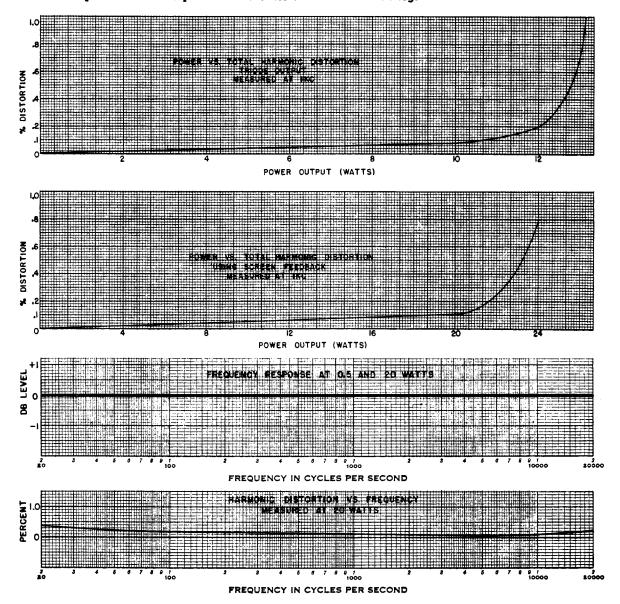- Bias: Adjust R₁₉ for 36 volts D.C. at point "A". This will give a total cathode current of about 112 ma, for the output stage.
- 2. D.C. Balance: Insert milliameter alternately in the cathode leads of V_3 and V_4 adjusting R_{21} for equal currents.
- A.C. Balance: Connect a sensitive A.C. voltmeter to point "A" and feed a signal into the amplifier. Adjust R₁₀ for minimum meter reading.



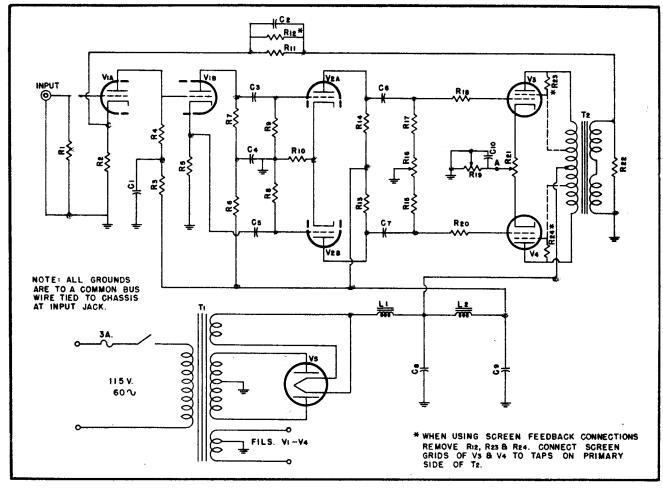CIRCUIT DIAGRAM OF THE FREED HI-FI AMPLIFIER



PARTS LIST

n	Ð	R	470KO	1	*******	CARRON	RESISTORS
n.,	n.	n.	- 4/UA\\.	1	watt	CARBON	TESIS I ORS

 R_2 , R_{10} = 470 Ω , 1 watt CARBON RESISTORS

 R_3 , R_5 , R_6 , R_7 =20K Ω , 1 watt CARBON RESISTORS

 R_{i} , $R_{i,i}$, $R_{i,i}$ =47K, 2 watt CARBON RESISTORS

 $R_{11} = 6.800\Omega$, 1 watt CARBON RESISTORS

 $R_{12} = 15K\Omega$, 1 watt CARBON RESISTOR (REMOVE WHEN USING SCREEN TAPS ON T₂)

 R_{15} , $R_{17} = 120K$, 1 watt CARBON RESISTOR

 $R_{16} = 50 K\Omega$, 2 watt CARBON POTENTIOMETER

 R_{1N} , R_{2n} = 1000 Ω , $\frac{1}{2}$ watt CARBON RESISTOR

 $R_{19} = 400\Omega$, 10 watt wirewound RESISTOR, ADJUSTABLE

 $R_{21} = 50\Omega$, 2 watt CARBON POTENTIOMETER

 $R_{\rm 20}~R_{\rm 21}$ =1000, 1/2 watt CARBON RESISTORS (USED WITH TRIODE OUTPUT PLATE TO SCREEN GRID)

C₁, C₄ =20 mf, 450 volt ELECTROLYTIC CAPACITORS

C₃, C₅ = .22 mf, 400 volt, MOLDED PAPER CAPACITOR

C₆, C₇ = .47 mf, 400 volt, MOLDED PAPER CAPACITOR

C₂ = 50 mmf MICA CAPACITOR

C_s, C_n = 20 mf, 500 volt ELECTROLYTIC CAPACITORS

T₁ = FREED KP-10 POWER TRANSFORMER

T₂ =FREED KA-10 OUTPUT TRANSFORMER

=CONNECTED 16 ohm SECONDARY

 $L_{_1}$ =FREED KC-10 FILTER REACTOR

L₂ = FREED KC-11 FILTER REACTOR

 V_1 , $V_2 = 6SN7-GT$

 V_3 , $V_4 = 5881$

 $V_s = 5U4-G$

C₁₀ = 100 mf, 50 volt ELECTROLYTIC CAPACITOR

FREED TRANSFORMER CO., INC., 1718 WEIRFIELD ST., BROOKLYN 27, N. Y.