

1. Summary

Valve PA Amplifier. \$103 eBay July 2009

Steane's Sound Systems Pty Ltd. Model M265.

Microphone and Pickup inputs via 8-pin octal connectors (1 removed). Microphone input direct to 6C6 grid in pentode configuration gain stage to microphone volume pot. Pickup input direct to volume pot. MIC and PU signals from pots are summed and taken to input of 6C6 triode configuration gain stage with output to MUSIC Tone pot and 6SN7 self-balancing paraphase splitter. Push-pull 6V6GT pentode output to 1K PP to 8ohm transformer. HT supply from full-wave centre-tapped transformer using 5V4G diode rectifier and series resistor-choke to cap.

The OT has been changed, as the chassis shows signs of having had different mounted parts (XM392 used a 1981 model OT). Two resistors and PP stage bypass cap are 'modern'. The input 6C6 screen bypass 0.1uF cap has been moved to the cathode (?). The banana plugs appear to be add-ons. A quality inspection label is mostly gone – can see Wired, Inspected, Tested, Passed, with signatures. Tag with "ANSETT A.N.A. BHF 34-2" added.

Output Transformer	TU206 12000 (12K PP, 8Ω output).
Power Transformer	1498, Dated XX NOV 1948.
Choke 1	18H at 45mA, 21ΩDC , Dated 23 Nov 1948
Valves	5V4G – no other markings – loose end 6V6GT Miniwatt J22 D↑D 6V6GT Radiotron 19 HF 6SN7GT Radiotron – cracked base 6C6 Radiotron (loose top) 6C6 Philips ?6
POTs	2x IRC 0.5MEG/C, 17209/34, 106051. 1x Morganite 500k Log; S.057 BJ
Caps	Ducon Aerovox EE 10577 8uF 600V x3; Ducon 16uF 525V x1: Ducon ET 10769 (code SM58)

Condition:

Surface rust on base plate and on mounting hardware and transformer frames. OT has been changed (other fittings drilled) - present OT probably 6-10W – TU206 (it's not Rola). Possibly 200R added to 250R 5W Merlin. All grommets for wire pass through and preamp valve shock mount are hardened. All electrolytic aesthetically look fine, but are very old. Changed pot. 1x 6C6 and 1x 6V6 faulty.






2. Modifications

- Megger tested power transformer and choke. Check heater voltage versus primary taps.
- Disconnect HT electrolytics, but leave chassis mounts in place.
- Remove banana sockets. Insert Speakon connector in octal base cutout.
- Added input socket on front panel. Added 10k grid stopper to V1.
- Lower grid-stopper of V2 6C6 triode to 100k. Add 100k grid-stopper to PI input.
- Moved Pickup pot to pre-PI. Moved tone to work with Pickup pot aka Marshal 18W tone.
- Replaced the power cable and faulty Tone pot.

- Add 10R 6V6 cathode current sense resistors, and wired sense leads to rear panel octal.
- Changed 6V6 grid stoppers to 10k.
- Add mains switch, fuse, 275VAC MOV to primary. Added 0.4A fuse to PT secondary CT.
- Added 4k7/350VDC MOV-R protection to OT primary.
- Added heater humdinger pot.
- Removed resistor in series with choke. Added snubber capacitor before choke. VS1 should be about 330V – use 400V rated caps.
- Added neoprene washers to either side of valve base to increase compliance.
- Replaced in-situ OT with A&R OT916-8; 8k5 UL with 8Ω output; High fidelity range suited to 6V6. Similar UL designs for 6V6:
 - Acro TO-310 OT, 8k PP, 10W hi-fi
 - Radiotronics June 1955 paper on 6V6 UL by Langford Smith and Chesterman.

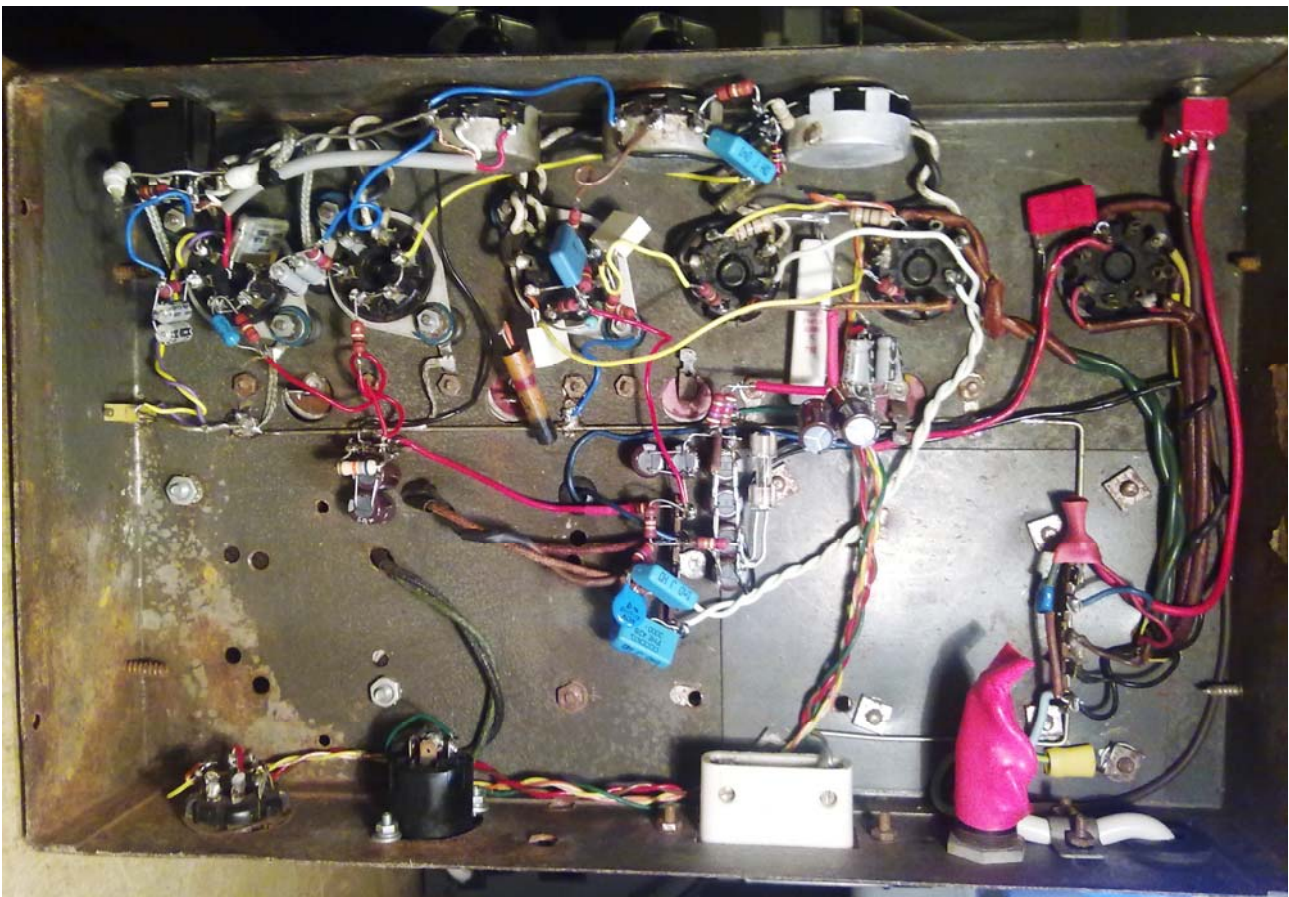Given the more modern 'Philips' style in a 1953 advert, and choke date of late 1948 – this amp is an earlier model circa 1949-50.



3. Steane's Sound Systems

The Powerhouse museum has a microphone from them, with a comment about them being in Melbourne, and then Sydney in 1940-60's.

They are identified in The Argus in October 1943, and again in 1945 at 290 Exhibition St, Melbourne.

There are adverts in the April 1949 Canberra times for "Stanes Sound Systems" who do PA's and sound for venues.

Many adverts in Radio & Hobbies from Sept 49 to Dec 1955, with addresses for 60-80 Miller St Melb ¹, and 367 Kent St Sydney ², and many state and NZ outlets (eg. Lawrence & Hanson, and Homecrafts) focussing on sound reproduction equipment. 1953 advert shows similar casing amplifier with ratings available of 13W, 30W and 70W, and four pots – a close descendant.

They had associated trading names of BRODERS PTY LTD and UNITED ELECTRONIC SERVICING PTY LTD, and became a registered company in 1931 and deregistered in 1999. They used a distinctive SSS badge on the amp I have.



**STEANE'S
AMPLIFIERS** (as illustrated)

13 WATTS AC	-----	£48/16/2
30 WATTS AC	-----	£54/14/5
70 WATTS AC	-----	£85/18/9
13 WATTS 6 or 12 V DC		
and 240 V AC	-----	£54/3/-



1953 advert in Radio & Hobbies

Graham Scott,
154 Russell St
Toowoomba, QLD 4340
07 4632 4109

4. Measurements

Voltage rail regulation.

Rail	Idle (Wurlitzer OT)	Idle A&R OT 916 UL	Max output
VS1	305V (peaks to 370V), 850mVrms ripple	300V	297V
VS2	240V		
VS3	195V		
Cathode	18.5V (27mA + 27mA) 8W 330R	18.5V (36+38mA) 250R	
Heater 1	6.4V		
Heater 2			
Sec HT	385+385V		

12VAC 50Hz nominal applied to TU206 output transformer (this was replaced by Wurlitzer and the A&R OT 916-8)

Winding	Voltage rms	Turns ratio; Impedance for 12K pri; Spec level; Notes
Pri P-P: BLU to BRN	415	
Sec: GRN to GRN	11.27	36.8; 8.9 Ω; Appears reasonable for 12K PP

Output transformer primary DC resistance: 420Ω plate-to-plate.

¹ Now Basso Project Management. Miller St is near northern section of Spencer, between Victoria and Abbotsford. Used by Briginshaw Bros in 1942.

² Now Casablanca Media Corp. Located in central section.

Power transformer primary DC resistance: 21Ω , 0-240V.

Power transformer secondary DC resistance: $103+112\Omega$, 400-0-400V.

Choke: 21Ω dc resistance; 18H at 46mADC; 14H at 95mADC.

23mVrms output noise in to 17 ohm load with pots at full level and no input (shorted at socket).

12Vrms output at start of clipping (8W) with Wurlitzer OT. Clipping is pretty symmetric, but un-driven side of PI then starts to get a scalloped dip at 10W, which is then max output level. Perhaps change PI for long-tail pair config.

Tone control interacts with signal level – and loading of 6C6 is not symmetric so filter response is unbalanced. Coupling caps reduced to allow tone control to roll off bass. Perhaps change to?

Large hum pickup from open 6C6, but this is reduced to negligible level with standard shell metal screen fitted.

VS1 idles at 310V, and droops to 300V at full load. Screen voltage sags to 280V (effectively 260V to cathode) at full load – tweaked by reducing dropper to 2k4. Check design – may need to modify VS2, VS3.

To do: guitar check; update this doc.

5. Design Info

5.1 Input Gain Stage

Pentode connected 6C6 gain stage. Effective signal output resistance is 270k // 500k // 1M ~ 150K. The 6C6 characteristic curves are same as for 6J7, and using 6J7 datasheet tables for resistance coupled amplifier configuration with:

VS3=300V, RL=250k, Rg=500k, Rc=1k2, Rd=1.2M, gives a gain of 140.


VS3=180V, RL=250k, Rg=250k, Rc=1k2, Rd=1.1M, gives a gain of 93.

In-circuit measurement is RL=270K, Rd=1M, and Rg~330k (500K//1M). For lower VS3, the gain will reduce. Rc and Rd screen should be bypassed – note - bypass on screen moved ???.

RESISTANCE-COUPLED AMPLIFIER CHART

- C = Blocking Condenser (μ f)
- Cc = Cathode By-Pass Condenser (μ f)
- Cd = Screen By-Pass Condenser (μ f)
- Ebb = Plate-Supply Voltage (Volts)
- Eo = Voltage Output (Peak Volts)
- Rc = Cathode Resistor (Ohms)
- Rd = Screen Resistor (Megohms)
- Rg = Grid Resistor (Megohms)
- RL = Plate Resistor (Megohms)
- V.G. = Voltage Gain

RESISTANCE-COUPLED PENTODE AMPLIFIER

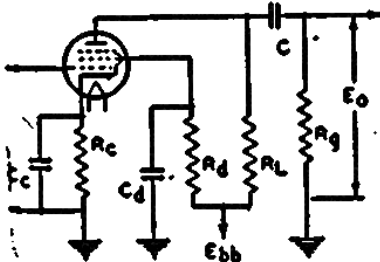

Condensers C, Cc, and Cd have been chosen to give output voltages equal to 0.7 Eo for fi of 100 cycles. For any other value of fi multiply values of C, Cc, and Cd by 100/fi. In the case of condenser Cc, the values shown in the table are for an amplifier with d-c heater excitation; when a.c. is used, depending on the character of the associated circuits, the gain, and the value of fi, it may be necessary to increase the value of Cc to minimize hum disturbances. It may also be desirable to have a d-c potential difference of approximately 10 volts between heater and cathode. The voltage output at fi for n like stages equals (0.7 Eo)n. For an amplifier of typical construction, approximate values of fi for different values of RL are: 0.1 meg., 20000 cps; 0.25 meg., 10000 cps; 0.5 meg., 5000 cps.

6J5, 6J5-G, 6J5-GT: See 6F8-G.

6J7, 6J7-G, 6J7-GT, 6W7-G, 12J7-GT, 6C6, 57: As triodes, see 6C5:

Ebb ¹	90			180			300				
	0.1	0.25	0.5	0.1	0.25	0.5	0.1	0.25	0.5		
Rg ²	0.25	0.5	1	0.25	0.25	0.5	1	0.25	0.5	1	
Rd	0.44	1.18	2.6	0.5	1.1	1.18	1.4	2.9	0.5	1.18	2.9
Rc	1100	2600	5500	750	1200	1600	2000	3100	450	1200	2200
Cd	0.05	0.03	0.05	0.05	0.04	0.04	0.04	0.025	0.07	0.04	0.04
Cc	5.3	3.2	2	6.7	5.2	4.3	3.8	2.5	8.3	5.4	4.1
C	0.01	0.005	0.0025	0.01	0.008	0.005	0.0035	0.0025	0.01	0.005	0.003
Eo ³	22	32	29	52	41	60	60	56	81	104	97
V.G. ⁴	55	85	120	69	93	118	140	165	82	140	350


Modified to triode stage with relatively low stage gain ~15, but total amp gain was too low, so reverted to pentode mode with 680R cathode, 100k anode load, and 470k screen.

5.2 2nd Gain Stage

Triode connected 6C6 gain stage. Supply voltage about 250V; effective signal load resistance is 100k//470k//pot; and cathode resistor is 1K5. The plate voltage Vp axis intercept is 250V for no plate current, and the plate current Ip axis intercept is 250V / 101KΩ = 2.5mA. The gate-cathode voltage (Ec on the graph) operating point is at Vgc=1.5Kx2.5mA = 3.7V, and varies with plate current through the 1k5Ω gate-cathode resistance with the characteristic shown on the graph as a line passing through Ip=3.5mA for Vgk=-5V, and through Ip=6mA for Vgk=-10V. The intersection of the two lines is the nominal biased operating point.

The input voltage swing limit is from the bias point at $V_{gk} = -3.7V$ and so is fairly unsymmetrical.

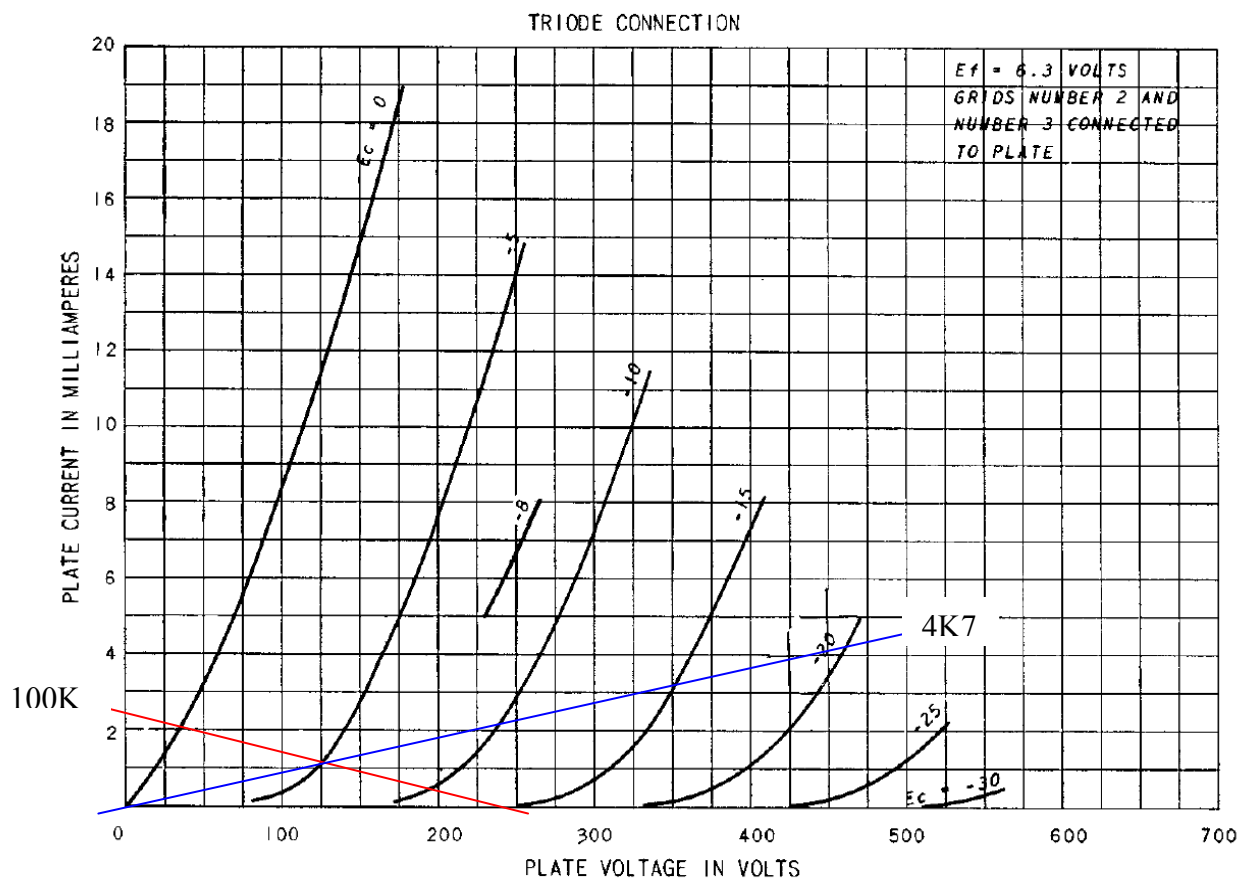
The triode connection tables in RCA manual suggest an $R_c \sim 4k7$ to $5k6$, which should achieve a better symmetry – and the gain is about 12.



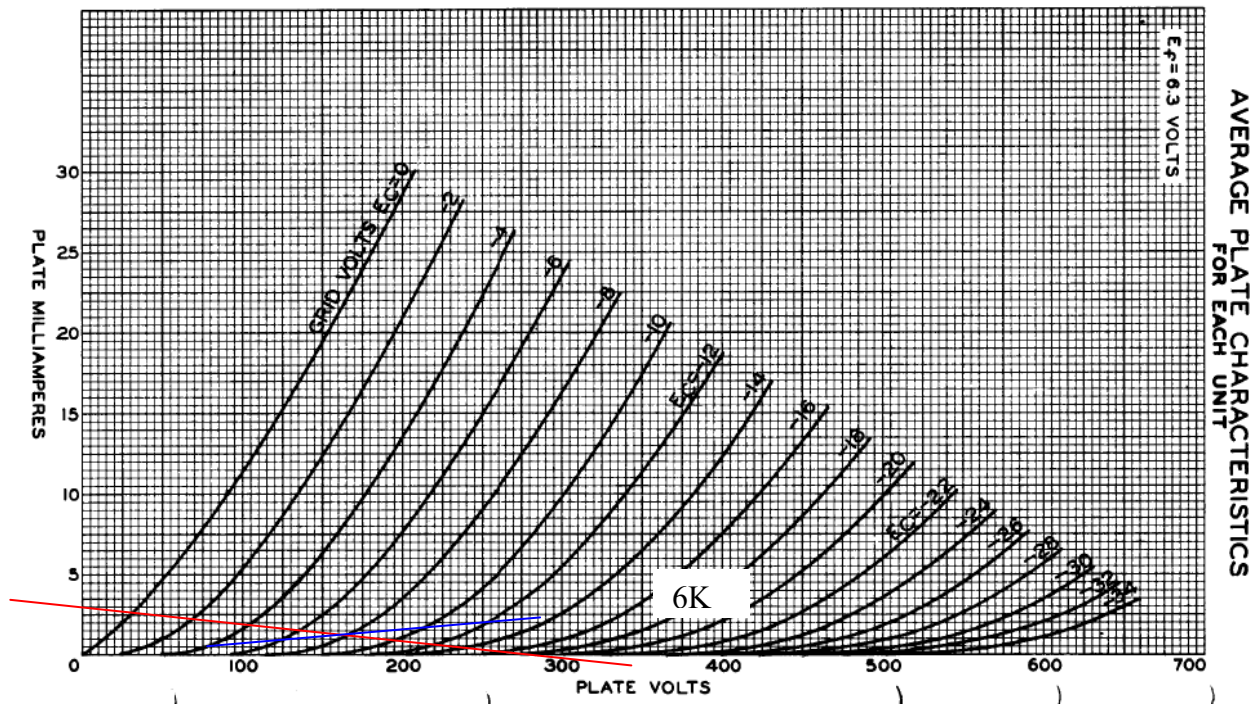5.3 Splitter stage

A see-saw floating self-balancing paraphase splitter circuit using a 6SN7. Driven by 6C6 so drive impedance is different for each 6SN7 triode. Gain of 6SN7 indicates imbalance may also be substantial. Cathode bias at about 8V and 1.1mA per 6SN7 triode, and anode voltage at $160+8=170V$ with a 100k load and 280V HT. Output impedances of each side are fairly similar as r_a of 6SN7 is quite low.

Paraphase gain is $\sim 1 + (1+1+1)/14 = 1.21$.



5.4 Output Stage

In this Class AB push-pull UL output stage, one 6V6 tube is pushed into conduction and the other tube is pulled into cutoff, and there is a region of overlap where both tubes conduct equivalent levels of current. The cathodes are biased with a common resistor to ground. The A&R OT 916-8 presents 8.5kΩ impedance plate-to-plate OPT for 8 ohm speaker, presents each tube with a 2.1kΩ load impedance for larger signal currents, and 4.2k loading for small signal levels.

Determining a suitable bias current level is not an empirical design approach, rather it is based on the following recommendations:

- Start with the lowest bias current possible (ie. most negative grid bias voltage), and based on listening tests, increase the bias current until the sound character is acceptable, but:
- use the lowest possible bias current level, as this generally increases the life of the tubes, and decreases the chance of operating at excessive plate dissipation; and
- keep the bias current level below 70% of the recommended design max plate dissipation (ie. <9W); and
- assess the dynamic loadline to see if it moves into region of increased plate dissipation.

As the output loading increases, the supply voltage VS1 sags only a few volts from 305V, due to supply regulation. Plate DC voltage will be lower than VS1 by an amount up to ~40V; ie. OPT half resistance of about 200Ω with a peak current of up to about 0.1A, and cathode bias of 20V.

The screen voltage will correspondingly sag. Screen current level increases as Vg approaches 0V, possibly to over 40mA, with an additional drop across the screen stopper resistor. Screen voltage needs to sag to about 250+20=270V at start of overdrive to nominally operate in to knee.


The maximum output valve bias current allowed is dependant on the maximum recommended plate dissipation of 12W for the 6V6: $I_{bias(max)} = P_d / V_b = 12W / 300V = 40mA$. $I_{bias(nom)} = 0.7 \times 12W / 300V = 28mA$.

Assessing the 6V6 plate curves, which show 12W constant power contour, indicates how the plate will start at quiescent level of 27mA (V1=300V).


The common cathode resistance is about $18V / (27mA + 27mA) = 330\Omega$ at 1W.

The nominal output power of the amplifier will then be:
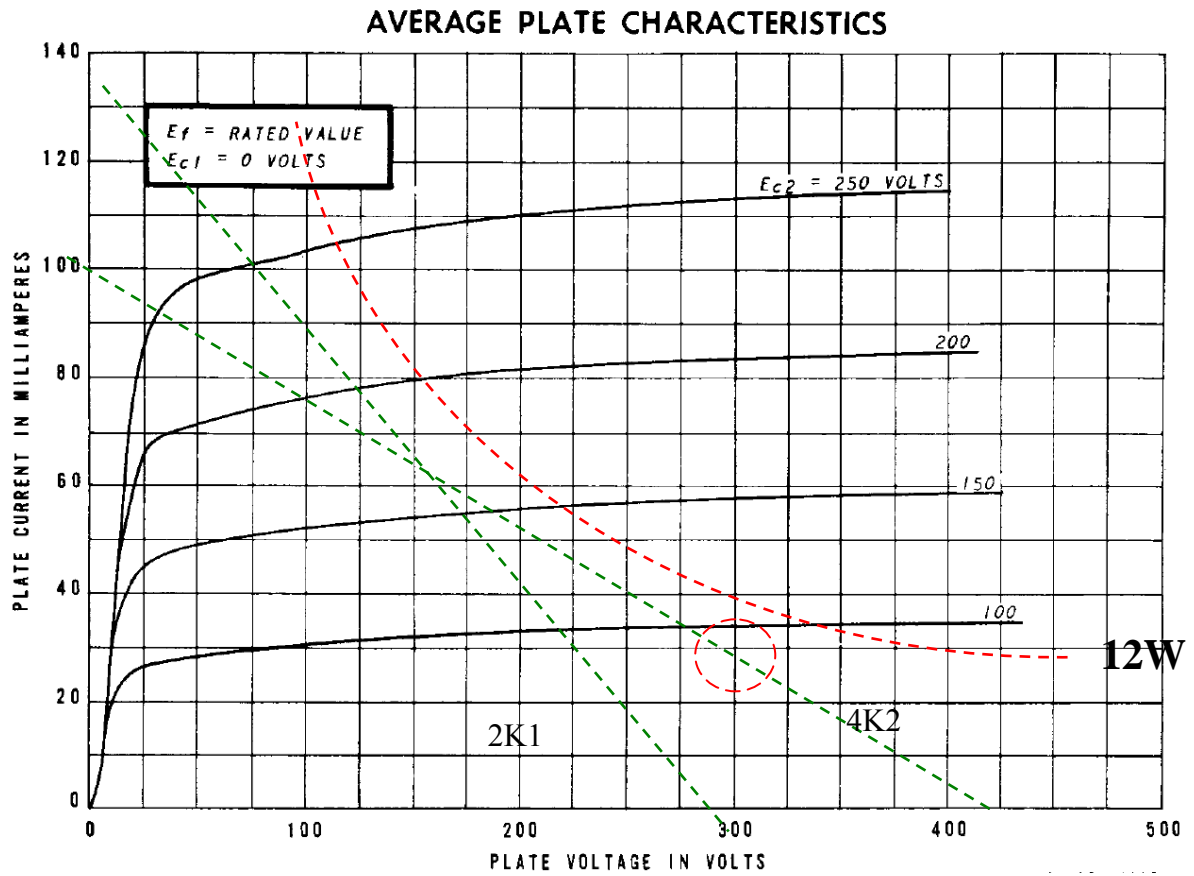
$$(I_{max})^2 \times R_{pp} / 8 = 0.09 \times 0.09 \times 8.5k / 8 = 8.5W$$






AVERAGE PLATE CHARACTERISTICS

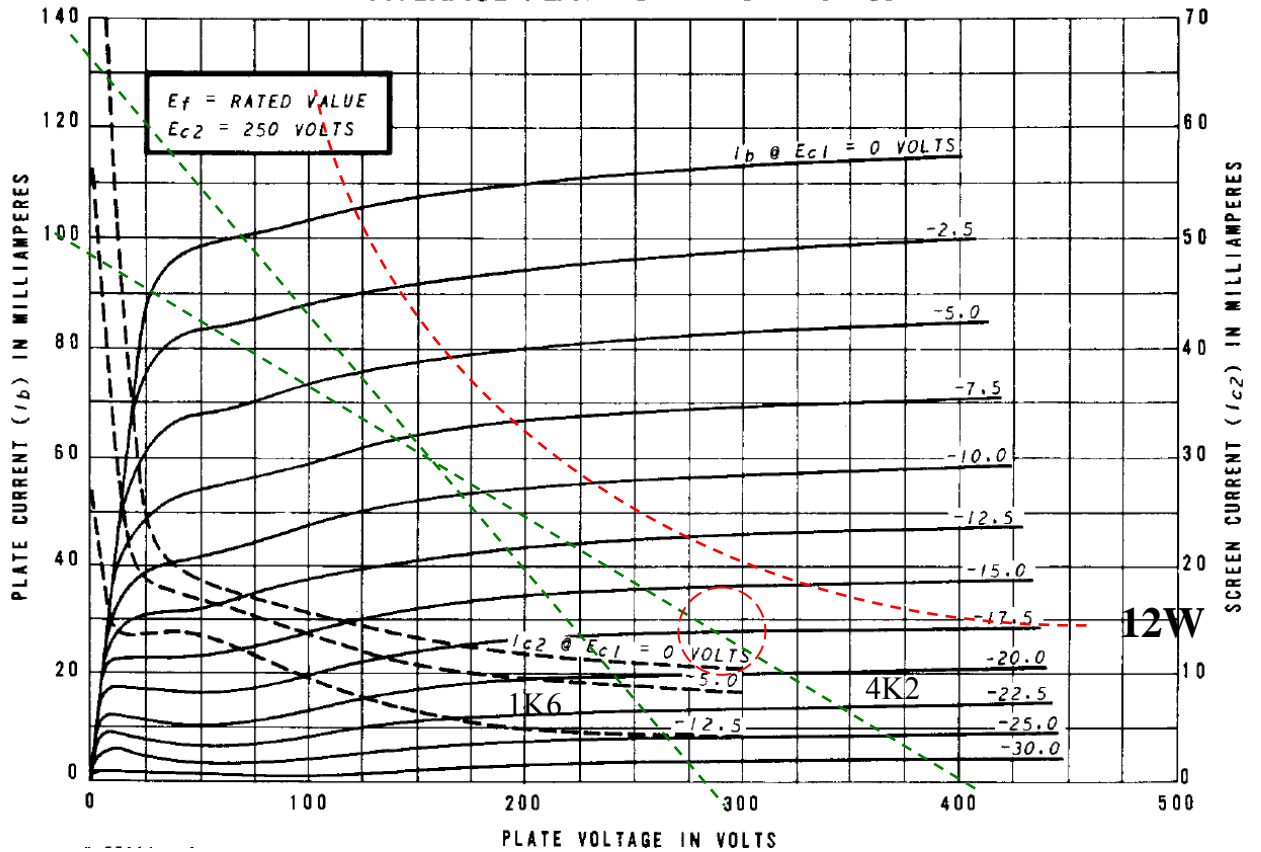

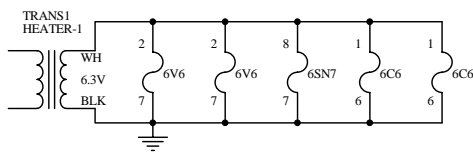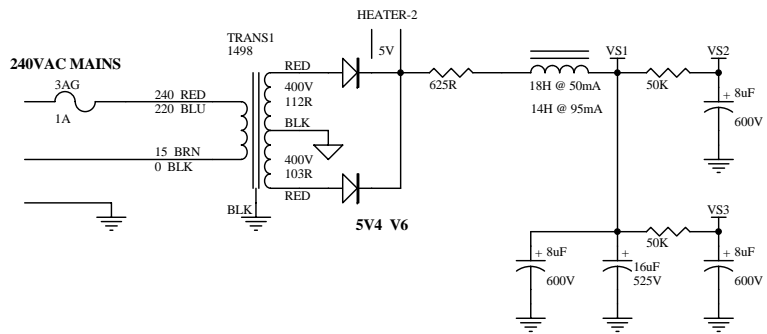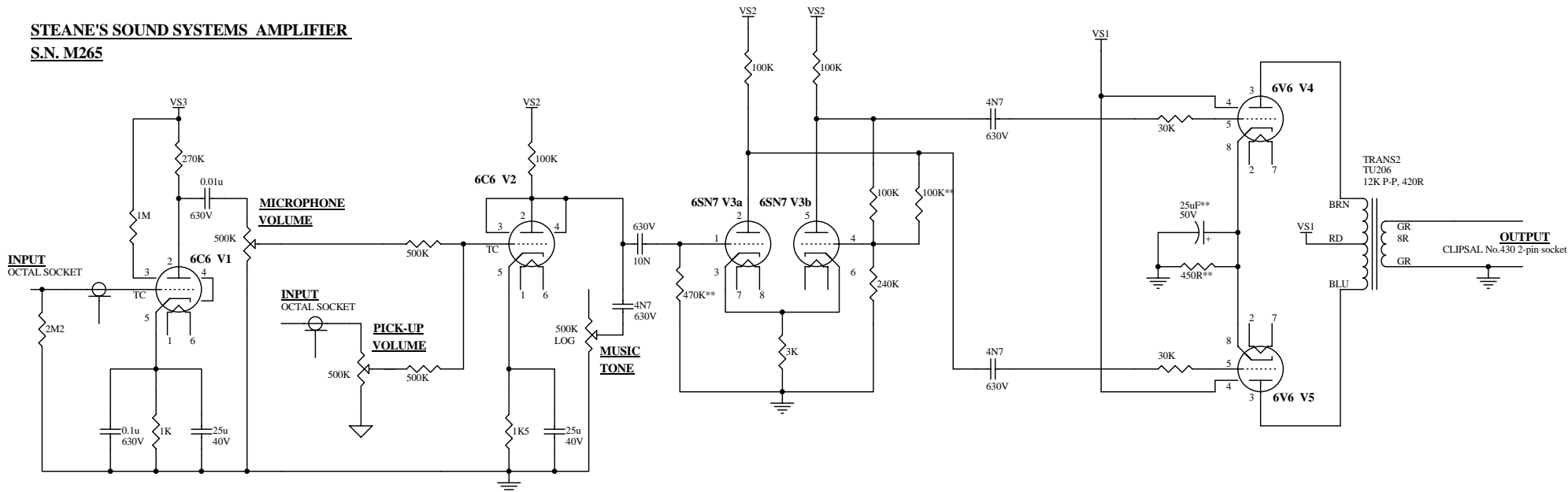
5.5 Power Supplies

The power supply is typical full-wave rectified type using double diode 5V4 and a 400-0-400VAC centre-tapped secondary. With a choke input LC filter, this gives about 340VDC at low load, reducing by about 20V for the 5V4, and 2V for the choke DC resistance, and 62V for series R, at 100mA.

STEANE'S SOUND SYSTEMS AMPLIFIER
S.N. M265



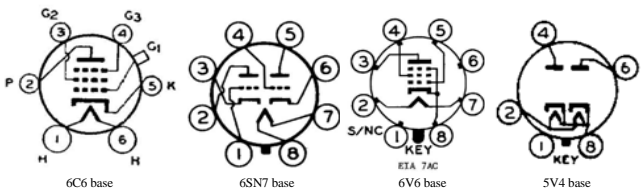Replacement Part **
 V1, V2, V3 on shock mount sockets
 ANSETT A.N.A. BHF 34-2 TAG






VOLTAGE RAILS		VALVE	QTY
RAIL	NO LOAD		
VS1	V	6C6	2
VS2	V	6SN7	1
VS3	V	6V6	2
HEATER-1	V	5V4	1
HEATER-2	V		




Title		
Size	Number	Revision
Date:	4-Aug-2009	
File:	C:\Program Files\Design Explorer 99 SE\Projects\Bbs amps\Amplifier Modules.dtb	

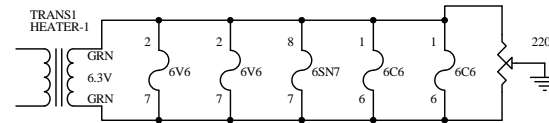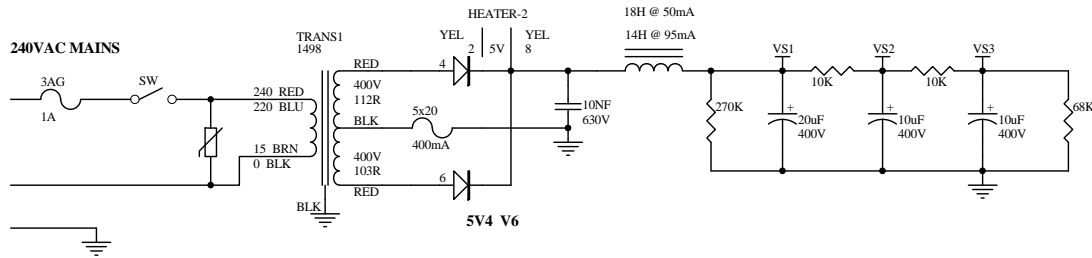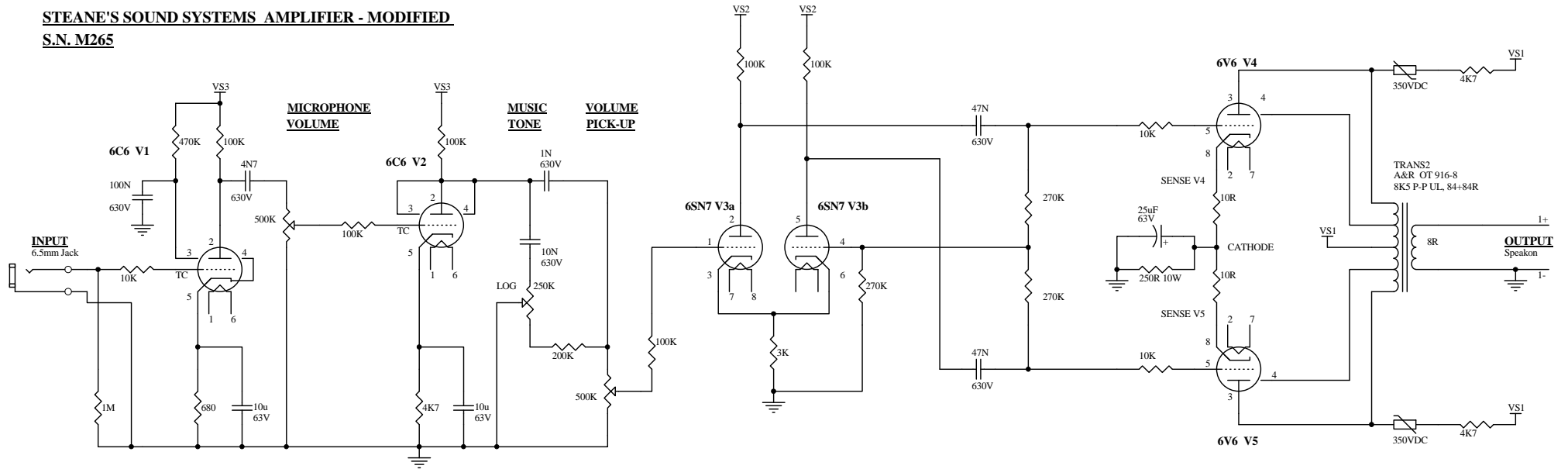
STEANE'S SOUND SYSTEMS AMPLIFIER - MODIFIED
S.N. M265



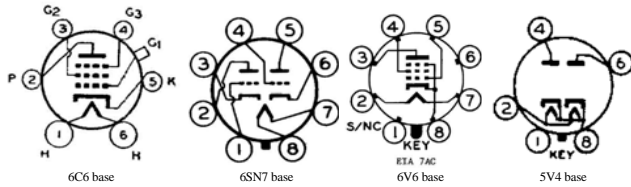V1, V2, V3 on shock mount sockets
 ANSETT A.N.A. BHF 34-2 TAG



VOLTAGE RAILS	NO LOAD	VALVE	QTY
VS1	310V	6C6	2
VS2	280V	6SN7	1
VS3	240V	6V6	2
HEATER-1	6.5V	5V4	1
HEATER-2	5V		
6V6 bias	36+36mA; 18.5V		

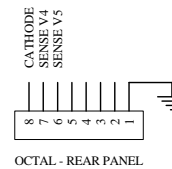

Title		
Size B	Number	Revision
Date: 29-Jul-2012	Sheet of	
File: \\sclient\C\Program Files\Design Explorer\90611\Projects\Amplifier Modules.ddb		